

PHY 211

Lecture 7 Notes

By

Dr. Ashraf Mousa Abdelwahed


Fall 2024

Chapter 6

Direct Current "DC" Circuits

➤ Resistors in series & parallel:

• Resistors in series:

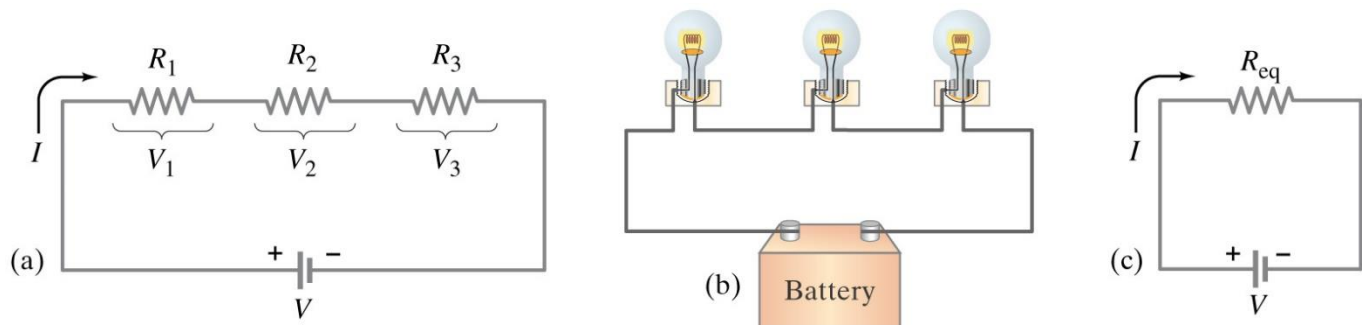

The same current I passes through R_1 , R_2 & R_3 .

The emf of the battery E is divided among the resistors

$$V_1 = IR_1 \quad V_2 = IR_2 \quad V_3 = IR_3$$

$$E = V_1 + V_2 + V_3$$

$$E = IR_1 + IR_2 + IR_3$$

$$E = I(R_1 + R_2 + R_3) \quad (1)$$

The equivalent resistance R_{eq} of $(R_1, R_2 \text{ & } R_3)$ will draw the same current I

$$E = IR_{eq} \quad (2)$$

From (1) & (2):

$$I(R_1 + R_2 + R_3) = IR_{eq}$$

$$\boxed{R_{eq} = R_1 + R_2 + R_3}$$


$$\boxed{R_{eq} > R_1 \quad \& \quad R_{eq} > R_2 \quad \& \quad R_{eq} > R_3}$$

$$\boxed{\frac{V_1}{V_2} = \frac{R_1}{R_2} \quad \& \quad \frac{V_1}{E} = \frac{R_1}{R_{eq}}}$$

For n resistors of same value R in series:

$$\boxed{R_{eq} = nR}$$

- Resistors in parallel:**

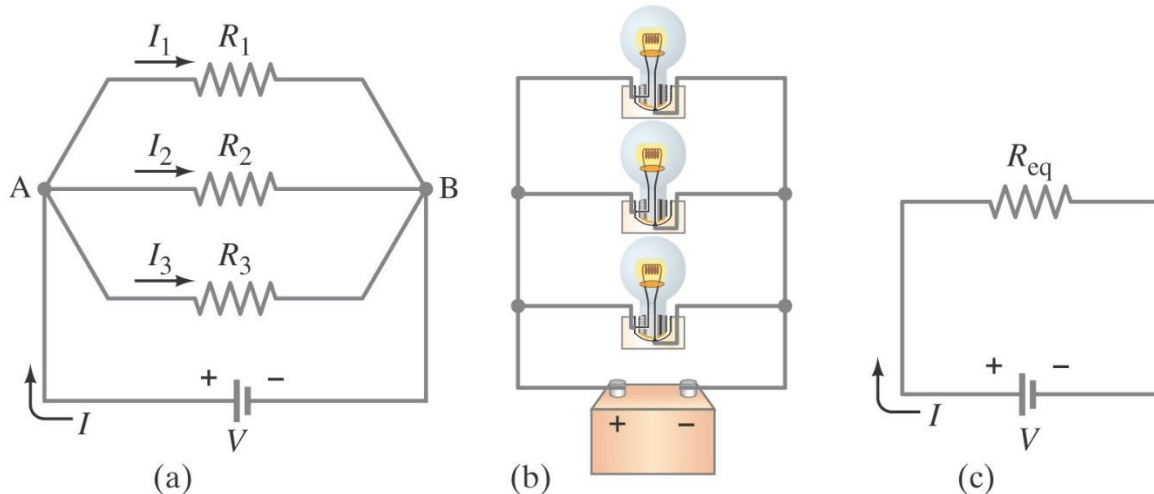

The voltage across R_1 , R_2 & R_3 will be the same and equal to E .

The current I will be divided through R_1 , R_2 & R_3 as I_1 , I_2 & I_3

$$I_1 = \frac{E}{R_1} \quad I_2 = \frac{E}{R_2} \quad I_3 = \frac{E}{R_3}$$

$$I = I_1 + I_2 + I_3 \rightarrow I = \frac{E}{R_1} + \frac{E}{R_2} + \frac{E}{R_3}$$

$$I = E \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) \quad (1)$$

The equivalent resistance R_{eq} of (R_1 , R_2 & R_3) will draw the same current I

$$I = \frac{E}{R_{eq}} \quad (2)$$

From (1) & (2):


$$E \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) = \frac{E}{R_{eq}}$$

$$\boxed{\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} \rightarrow \boxed{R_{eq} < R_1 \quad \& \quad R_{eq} < R_2 \quad \& \quad R_{eq} < R_3}$$

$$\boxed{\frac{I_1}{I_2} = \frac{R_2}{R_1} \quad \& \quad \frac{I_1}{I} = \frac{R_{eq}}{R_1}}$$

For n resistors of same value R in parallel: $\boxed{R_{eq} = \frac{R}{n}}$

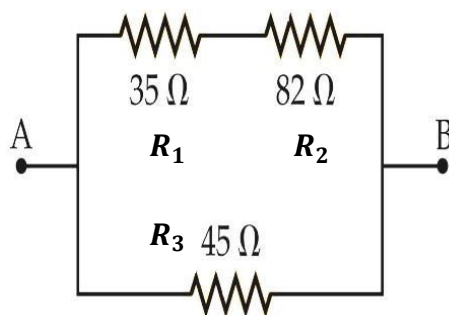- **Example 1:** Find the equivalent resistance between A and B for the group of resistors shown in figure below.



Solution

R_1 & R_2 are in series:

$$R_{12} = R_1 + R_2 = 35 + 82 = 117 \, \Omega$$

R_{12} & R_3 are in parallel:

$$\frac{1}{R_{eq}} = \frac{1}{R_{12}} + \frac{1}{R_3}$$

$$R_{eq} = \frac{R_{12} \times R_3}{R_{12} + R_3} = \frac{117 \times 45}{117 + 45} = 32.5 \, \Omega$$

- **Example 2:** A circuit consists of a 9.0-V battery connected to three resistors (42 Ω , 17 Ω and 110 Ω) in series. Find

- the current that flows through the battery and
- the potential difference across each resistor.

Solution

$$E = 9 \, V \quad R_1 = 42 \, \Omega \quad R_2 = 17 \, \Omega \quad R_3 = 110 \, \Omega$$

a)

$$I = \frac{E}{R_{eq}} = \frac{9}{42 + 17 + 110} = 0.053 \, A = 53 \times 10^{-3} \, A = 53 \, mA$$

b)

$$V_1 = IR_1 = 0.053 \times 42 = 2.226 \, V$$

$$V_2 = IR_2 = 0.053 \times 17 = 0.901 \, V$$

$$V_3 = IR_3 = 0.053 \times 110 = 5.83 \, V$$

- **Example 3:** A circuit consists of a battery connected to three resistors $65\ \Omega$, $25\ \Omega$ and $170\ \Omega$) in parallel. The total current through the resistors is 1.3 A . Find

(a) the emf of the battery and

(b) the current through each resistor.

Solution

$$I = 1.3\text{ A} \quad R_1 = 65\ \Omega \quad R_2 = 25\ \Omega \quad R_3 = 170\ \Omega$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{65} + \frac{1}{25} + \frac{1}{170} = 0.0612$$

$$R_{eq} = 16.34\ \Omega$$

a)

$$E = IR_{eq} = 1.3 \times 16.34 = 21.22\text{ V}$$

b)

$$I_1 = \frac{E}{R_1} = \frac{21.22}{65} = 0.33\text{ A}$$


$$I_2 = \frac{E}{R_2} = \frac{21.22}{25} = 0.85\text{ A}$$

$$I_3 = \frac{E}{R_3} = \frac{21.22}{170} = 0.12\text{ A}$$


➤ **EMF & terminal voltage:**

- When no current flows to an external circuit (open circuit), the potential difference between the terminals of the source is called the emf ($\mathcal{E}$)

$$V = \mathcal{E}$$

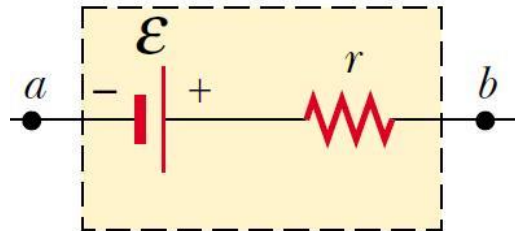

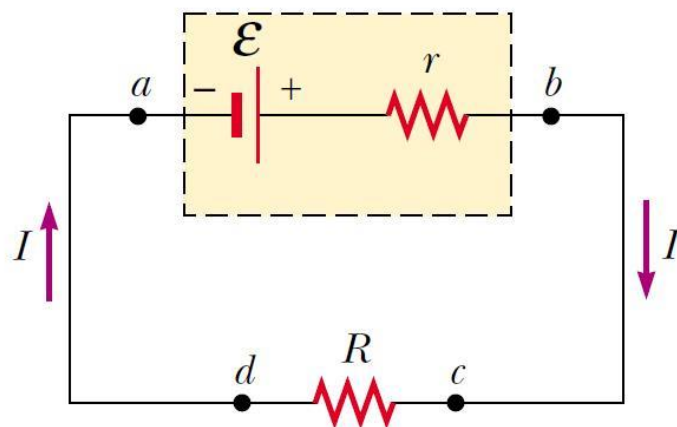- The potential difference between the terminals of the battery (V) when it is connected to a load is always smaller than the emf ($\mathcal{E}$) and is called the terminal voltage of the battery.



- When current flows through circuit, the terminal voltage is given by:

$$\boxed{V = \mathcal{E} - Ir}$$

r: internal resistance of battery

The voltage across R is:

$$V = IR$$

$$\mathcal{E} - Ir = IR \longrightarrow \mathcal{E} = IR + Ir \longrightarrow \mathcal{E} = I(R + r)$$

The current through the circuit is given by

$$\boxed{I = \frac{\mathcal{E}}{R + r}}$$

Example 4: car battery whose emf is 12.0 V and whose internal resistance is $0.010\ \Omega$. What is the terminal voltage when the current I drawn from the battery is (a) 10.0 A and (b) 100.0 A?

Solution

$$\text{a) } V = \mathcal{E} - Ir = 12 - (10 \times 0.01) = 11.9\text{ V}$$

$$\text{b) } V = \mathcal{E} - Ir = 12 - (100 \times 0.01) = 11\text{ V}$$

➤ EMFs in series & parallel:

I- EMFs in series

- It is used to increase the voltage obtained from source

$$V_{ab} = V_a - V_b = 3\text{ V} \quad (1)$$

$$V_{bc} = V_b - V_c = 3\text{ V} \quad (2)$$

(1) + (2) gives

$$V_{ac} = V_{ab} + V_{bc} = 6\text{ V}$$

$$V_{ac} = (V_a - V_b) + (V_b - V_c) = 6\text{ V}$$

$$V_{ac} = V_a - V_c = 6\text{ V}$$

$$\therefore V_a > V_c$$

So the current will flow from (a) to (c) into the external circuit (through R)

$$V_{ab} = V_a - V_b = -12\text{ V} \quad (1)$$

$$V_{bc} = V_b - V_c = +6\text{ V} \quad (2)$$

(1) + (2) gives

$$V_{ac} = V_{ab} + V_{bc} = -6\text{ V}$$



$$V_{ac} = (V_a - V_b) + (V_b - V_c) = -6\text{ V}$$

$$V_{ac} = V_a - V_c = -6\text{ V}$$

$$\therefore V_a < V_c$$


So the current will flow from (c) to (a) into the external circuit (through R)

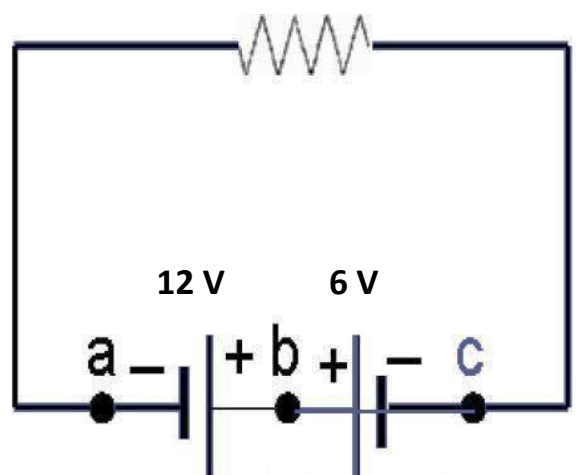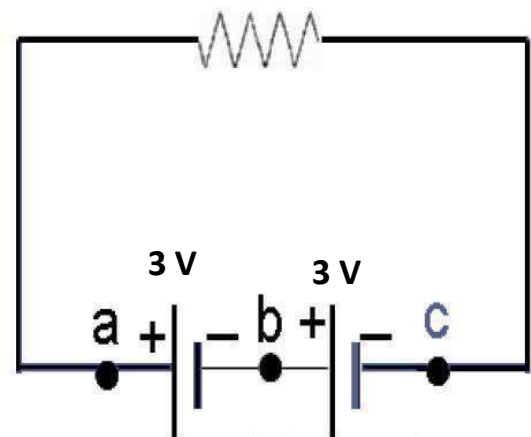- For batteries in series, the total internal resistance increase.



II- EMFs in parallel

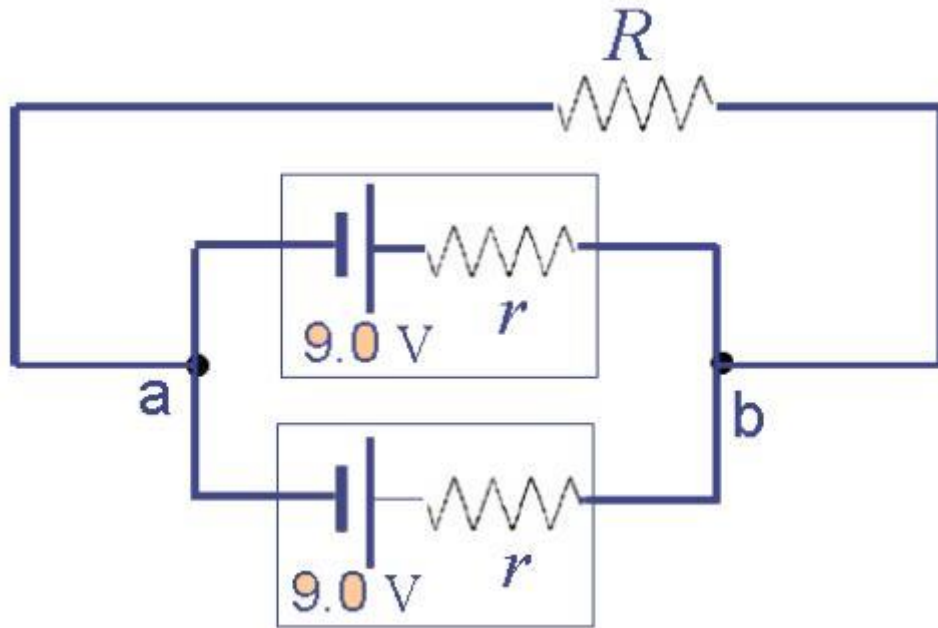- It is used to increase the current obtained from source




- The voltage is the same as one battery.
- Such an arrangement lasts twice as long as one cell because each of the sources has to produce only a fraction of the total current, and also the loss due to internal resistance is less than for a single cell (i.e. provides more energy).
- For batteries in parallel, the total internal resistance decreases.
- The internal resistance of the two batteries has to be the same, unless the battery with less internal resistance could be damaged due to reverse current.

➤ RC circuits:

1- Charging a capacitor

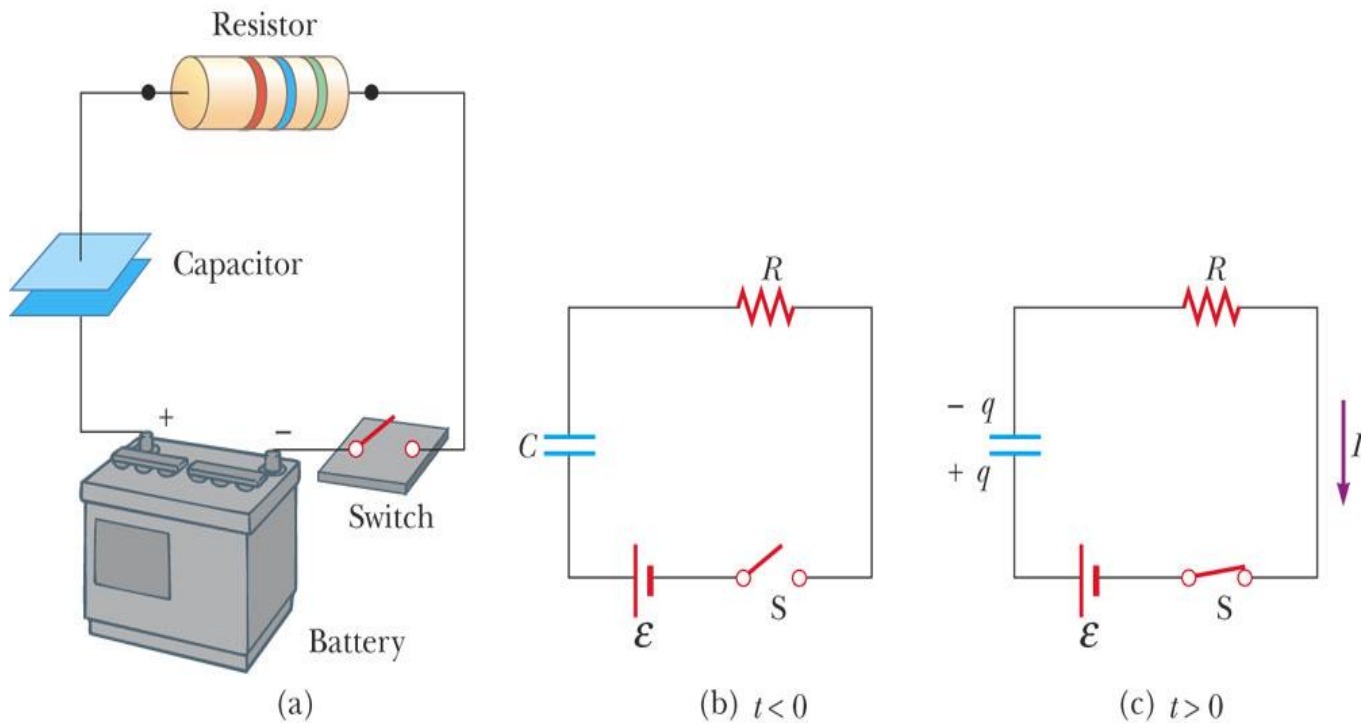- It is a circuit consisting of a battery of emf " $\mathcal{E}$ ", a resistance " R " & a capacitor " C " connected in series.



- When the switch " S " is closed, current will flow in the circuit and the capacitor will be charged.
- The charge $q(t)$ at any time (t) on the capacitor is given by

$$q(t) = q_o \left(1 - e^{-t/\tau}\right) = \mathcal{E}C \left(1 - e^{-t/\tau}\right) = \mathcal{E}C \left(1 - e^{-t/RC}\right)$$


q_o : maximum charge on the capacitor $q_o = \mathcal{E}C$

- The charge will start from zero till it reaches q_o .

τ : time constant of the circuit $\boxed{\tau = RC}$, it is the time required for the charge on the capacitor to reach (0.63) from its maximum value q_o while charging.

At $t = \tau$:
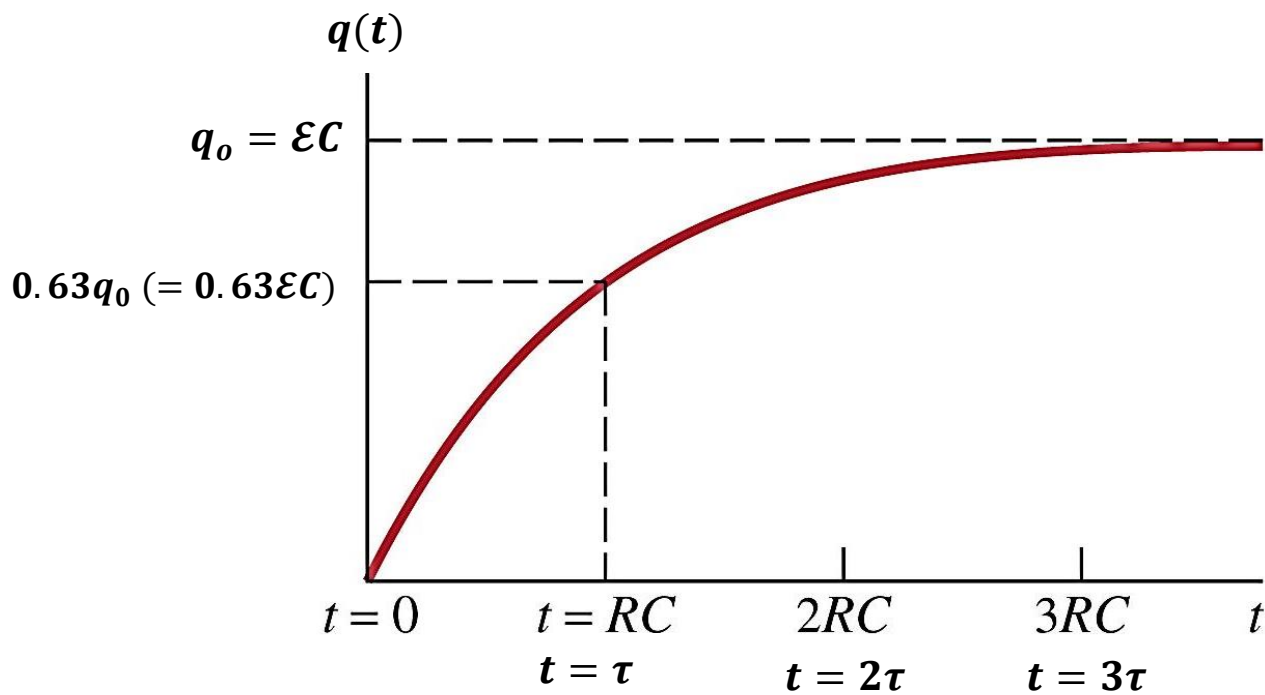
$$q(\tau) = q_o \left(1 - e^{-\tau/\tau}\right) = q_o (1 - e^{-1}) = q_o (1 - 0.37) = 0.63 q_o$$



The potential difference between the 2 plates of the capacitor at any time (t) is given by


$$V_C(t) = \frac{q(t)}{C} = \frac{q_o}{C} (1 - e^{-t/\tau}) \rightarrow \boxed{V_C(t) = \epsilon (1 - e^{-t/\tau})}$$

V_C starts from zero till it reaches ϵ .

τ : time constant of the circuit $\boxed{\tau = RC}$, it is the time required for the voltage across the capacitor to reach (0.63) from its maximum value ϵ while charging.

At $t = \tau$:
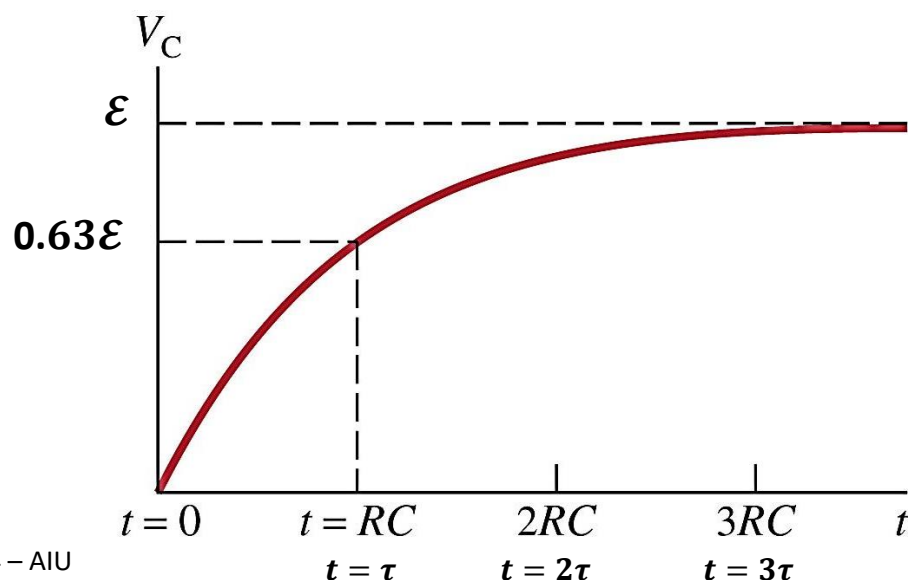
$$V_C(t) = \epsilon (1 - e^{-\tau/\tau}) = \epsilon (1 - e^{-1}) = \epsilon (1 - 0.37) = 0.63 \epsilon$$



The current at any time in the circuit is given by:

$$I(t) = I_0 e^{-t/\tau} = \frac{\mathcal{E}}{R} e^{-t/\tau}$$


I_0 : maximum value of current $I_0 = \frac{\mathcal{E}}{R}$

The current starts from I_0 and decays to zero.


τ : time constant of the circuit $\tau = RC$, it is the time required for the current to reach (0.37) from its maximum value " $I_0 = \mathcal{E}/R$ " while charging.

At $t = \tau$:
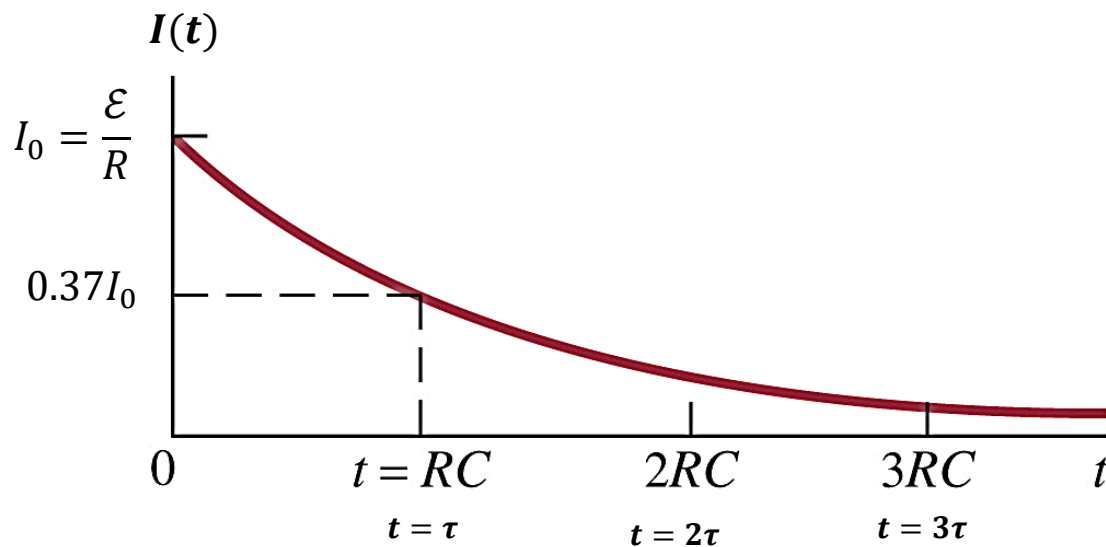
$$I(t) = \frac{\mathcal{E}}{R} (e^{-\tau/\tau}) = I_0 (e^{-1}) = 0.37I_0$$



2- Discharging a capacitor

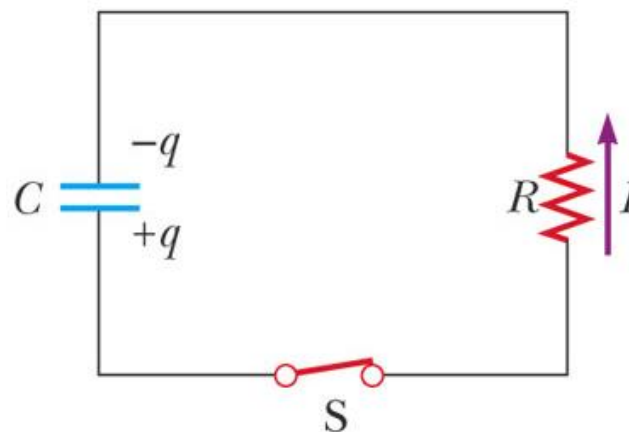

- If the battery is removed & the switch is closed, the capacitor will discharge its charge in the resistance.
- The charge $q(t)$ at any time (t) on the capacitor is given by

$$q(t) = q_0 e^{-t/\tau} = \mathcal{E}C e^{-t/\tau} = \mathcal{E}C e^{-t/RC}$$


q_0 : maximum charge on the capacitor $q_0 = \mathcal{E}C$

- The charge will start from q_0 till it reaches zero.

τ : time constant of the circuit $\tau = RC$, it is the time required for the charge on the capacitor to reach (0.37) from its maximum value while discharging.

At $t = \tau$:
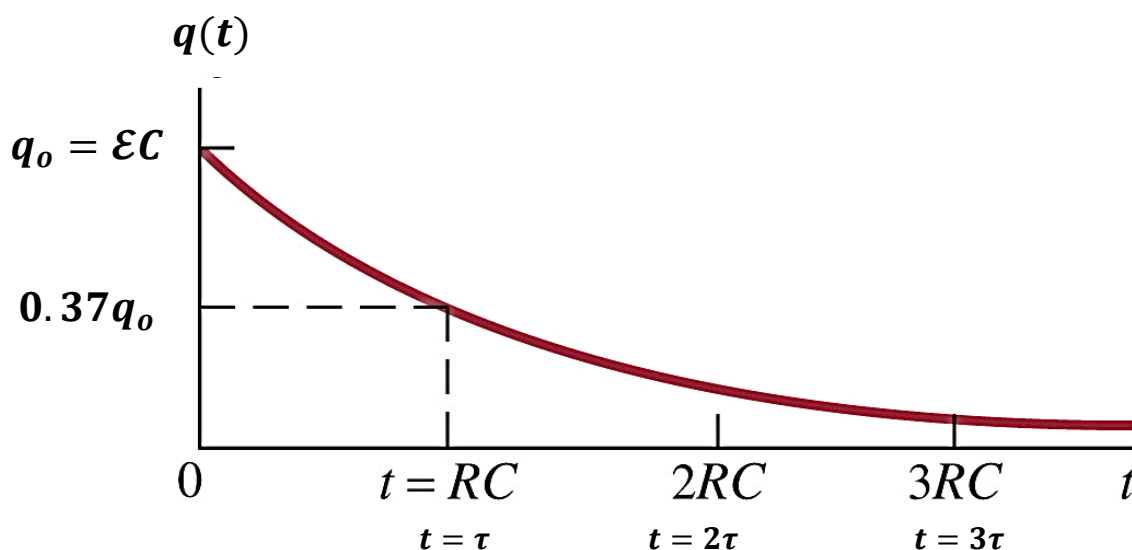
$$q(\tau) = q_0 e^{-\tau/\tau} = q_0 e^{-1} = 0.37 q_0$$



- The potential difference between the 2 plates of the capacitor at any time (t) is given by


$$V_C(t) = \frac{q(t)}{C} = \frac{q_0}{C} e^{-t/\tau} \rightarrow \boxed{V_C(t) = \mathcal{E} e^{-t/\tau}}$$

V_C starts from $\mathcal{E}$ till it reaches zero.

τ : time constant of the circuit $\tau = RC$, it is the time required for the voltage across the capacitor to reach (0.37) from its maximum value while discharging.

At $t = \tau$:
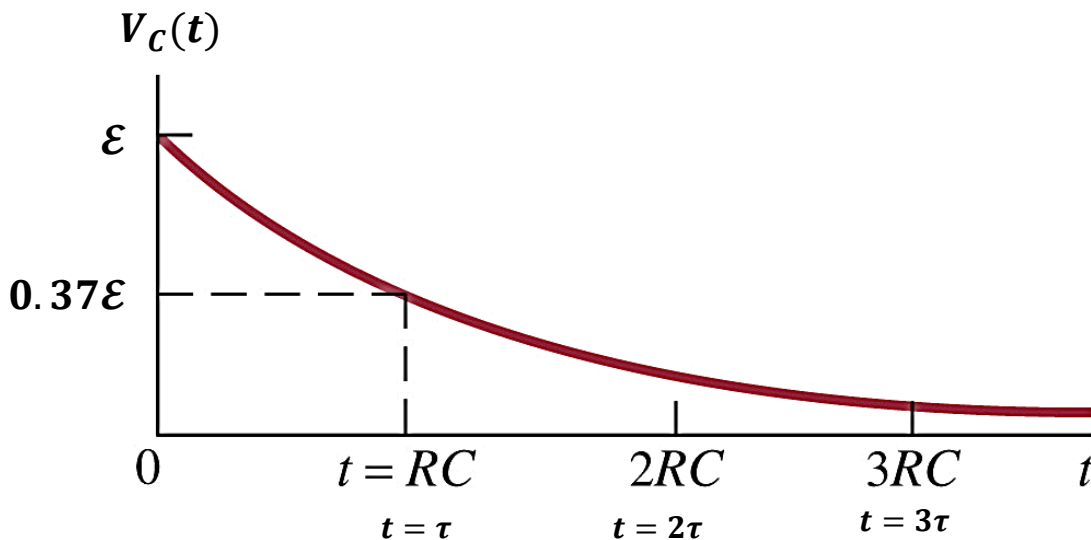
$$V_C(\tau) = \mathcal{E} e^{-\tau/\tau} = \mathcal{E} e^{-1} = 0.37 \mathcal{E}$$



- The current at any time in the circuit is given by:


$$\boxed{I(t) = I_0 e^{-t/\tau} = \frac{\mathcal{E}}{R} e^{-t/\tau}}$$

The current starts from I_0 and decays to zero.

τ : time constant of the circuit $\boxed{\tau = RC}$, it is the time required for the current to reach (0.37) from its maximum value " $I_0 = \mathcal{E}/R$ " while discharging.

At $t = \tau$:
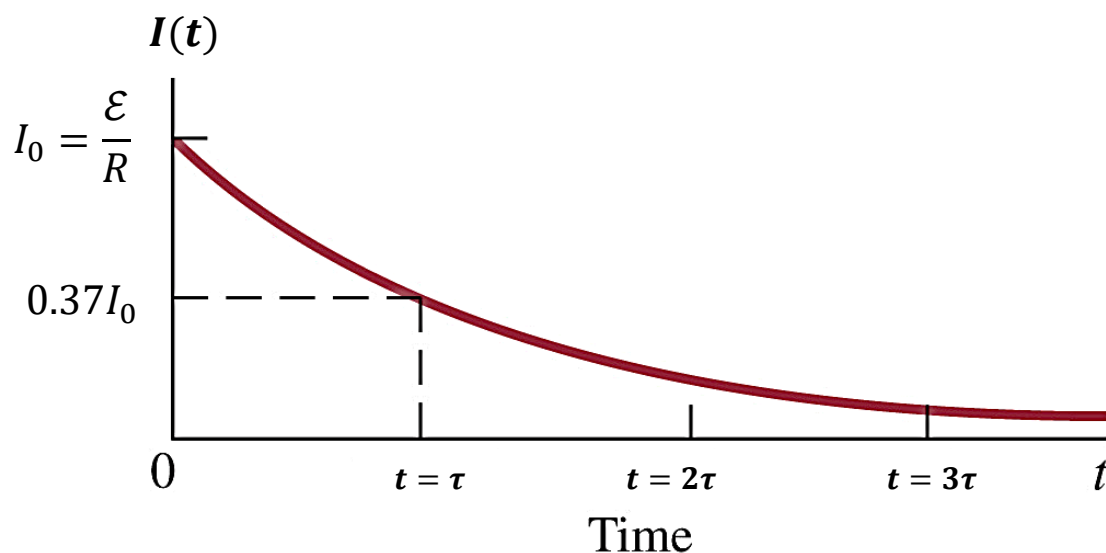
$$I(t) = \frac{\mathcal{E}}{R} (e^{-\tau/\tau}) = I_0 (e^{-1}) = 0.37 I_0$$



• **Example 5:**

The switch on an RC circuit is closed at $t = 0$. Given that $\mathcal{E} = 6 \text{ V}$, $R = 150 \, \Omega$ & $C = 23 \, \mu\text{F}$, how much charge is on the capacitor at time $t = 4.2 \text{ ms}$? & calculate the electric potential energy across the capacitor.

Solution

$$\because q(t) = q_o \left(1 - e^{-t/\tau}\right) = \mathcal{E}C \left(1 - e^{-t/\tau}\right) = \mathcal{E}C \left(1 - e^{-t/RC}\right)$$

$$q(4.2\text{ms}) = (6 \times 23 \times 10^{-6}) \left(1 - e^{\left(-4.2 \times 10^{-3} / (150 \times 23 \times 10^{-6})\right)}\right) = 97 \times 10^{-6} \text{ C}$$

$$U_c = \frac{qV_c}{2} = q \times \mathcal{E} \left(1 - e^{-t/\tau}\right) = \frac{97 \times 10^{-6} \times 6}{2} \left(1 - e^{\left(-4.2 \times 10^{-3} / (150 \times 23 \times 10^{-6})\right)}\right) = 2.05 \times 10^{-4} \text{ J}$$

• **Example 6:**

Consider an RC circuit with $\mathcal{E} = 12 \text{ V}$, $R = 175 \, \Omega$ and $C = 55.7 \, \mu\text{F}$. Find:

- The time constant of the circuit
- The maximum charge on the capacitor
- The initial current in the circuit

Solution

$$\text{a) } \tau = RC = 175 \times (55.7 \times 10^{-6}) = 9.75 \times 10^{-3} \text{ sec} = 9.75 \text{ ms}$$

$$\text{b) } q_o = \mathcal{E}C = 12 \times (55.7 \times 10^{-6}) = 6.68 \times 10^{-4} \text{ C}$$

$$\text{c) } I_o = \frac{\mathcal{E}}{R} = \frac{12}{175} = 0.068 \text{ A}$$